

Name: _____

Date: _____

Period: _____

Ohm's Law Quiz



Today you will be taking a quiz over Ohm's Law. Use your formula and do not forget to put your units

(Voltage = V, Current = A, Resistance = Ohm's)

1. If a toaster produces 15 ohms of resistance in a 150-volt circuit, what is the amount of current in the circuit?

V = _____ I = _____ R = _____

2. A cd player uses a standard 3 V battery. How much resistance is in the circuit if it uses a current of 0.05 A?

V = _____ I = _____ R = _____

3. How much voltage would be necessary to generate 7 amps of current in a circuit that has 20 ohms of resistance?

V = _____ I = _____ R = _____

4. A circuit contains a 1.5 volt battery and a bulb with a resistance of 6 ohms. Calculate the current.


V = _____ I = _____ R = _____

5. What resistance does a hair dryer have that is plugged into a 120 Volt circuit if it has a current of 4 amps going through it?


V = _____ I = _____ R = _____

6. _____ stays the same in a series circuit, and _____ stays the same in a parallel circuit.

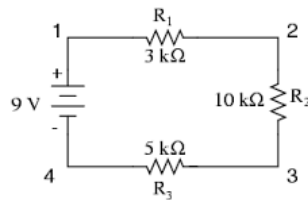7. Calculate the $R_t =$ ___ $I_t =$ ___ $I_1 =$ ___ $I_2 =$ ___ $I_3 =$ ___ $V_1 =$ ___ $V_2 =$ ___ $V_3 =$ ___ for the following circuit:



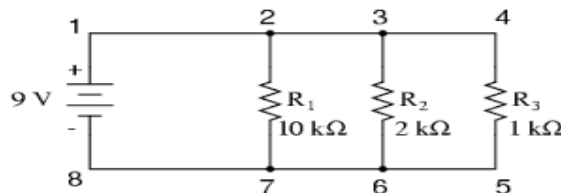8. Calculate the $R_t =$ ___ $I_t =$ ___ $I_1 =$ ___ $I_2 =$ ___ $I_3 =$ ___ $V_1 =$ ___ $V_2 =$ ___ $V_3 =$ ___ for the following circuit:




Name: _____

Date: _____

Period: _____

Ohm's Law Quiz

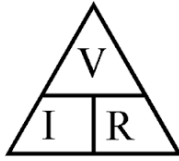

Today you will be taking a quiz over Ohm's Law. Use your formula and do not forget to put your units

(Voltage = V, Current = A, Resistance = Ohm's)

1. If a toaster produces 15 ohms of resistance in a 150-volt circuit, what is the amount of current in the circuit?

V = _____ I = _____ R = _____

2. A cd player uses a standard 3 V battery. How much resistance is in the circuit if it uses a current of 0.05 A?

V = _____ I = _____ R = _____

3. How much voltage would be necessary to generate 7 amps of current in a circuit that has 20 ohms of resistance?

V = _____ I = _____ R = _____

4. A circuit contains a 1.5 volt battery and a bulb with a resistance of 6 ohms. Calculate the current.


V = _____ I = _____ R = _____

5. What resistance does a hair dryer have that is plugged into a 120 Volt circuit if it has a current of 4 amps going through it?

V = _____ I = _____ R = _____

6. _____ stays the same in a series circuit, and _____ stays the same in a parallel circuit.

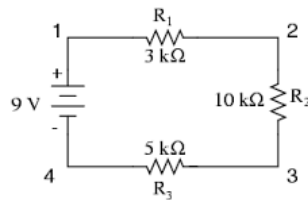7. Calculate the $R_t =$ ___ $I_t =$ ___ $I_1 =$ ___ $I_2 =$ ___ $I_3 =$ ___ $V_1 =$ ___ $V_2 =$ ___ $V_3 =$ ___ for the following circuit:



8. Calculate the $R_t =$ ___ $I_t =$ ___ $I_1 =$ ___ $I_2 =$ ___ $I_3 =$ ___ $V_1 =$ ___ $V_2 =$ ___ $V_3 =$ ___ for the following circuit:

